

Solar Professorsm



SolarProfessor.info



NABCEP – What you need to know

- Series vs. Parallel



Series vs. Parallel

Learning Objectives

- An understanding of series connections vs. parallel connections
- How to use with sample NABCEP Problems



Series vs. Parallel

Memorize the Rule...

In Series:

Volts ↑ (increase)

Amps = (stay the same)


In Parallel:

Volts = (stay the same)

Amps ↑ (increase)

Let's see it in action:

Batteries in Series

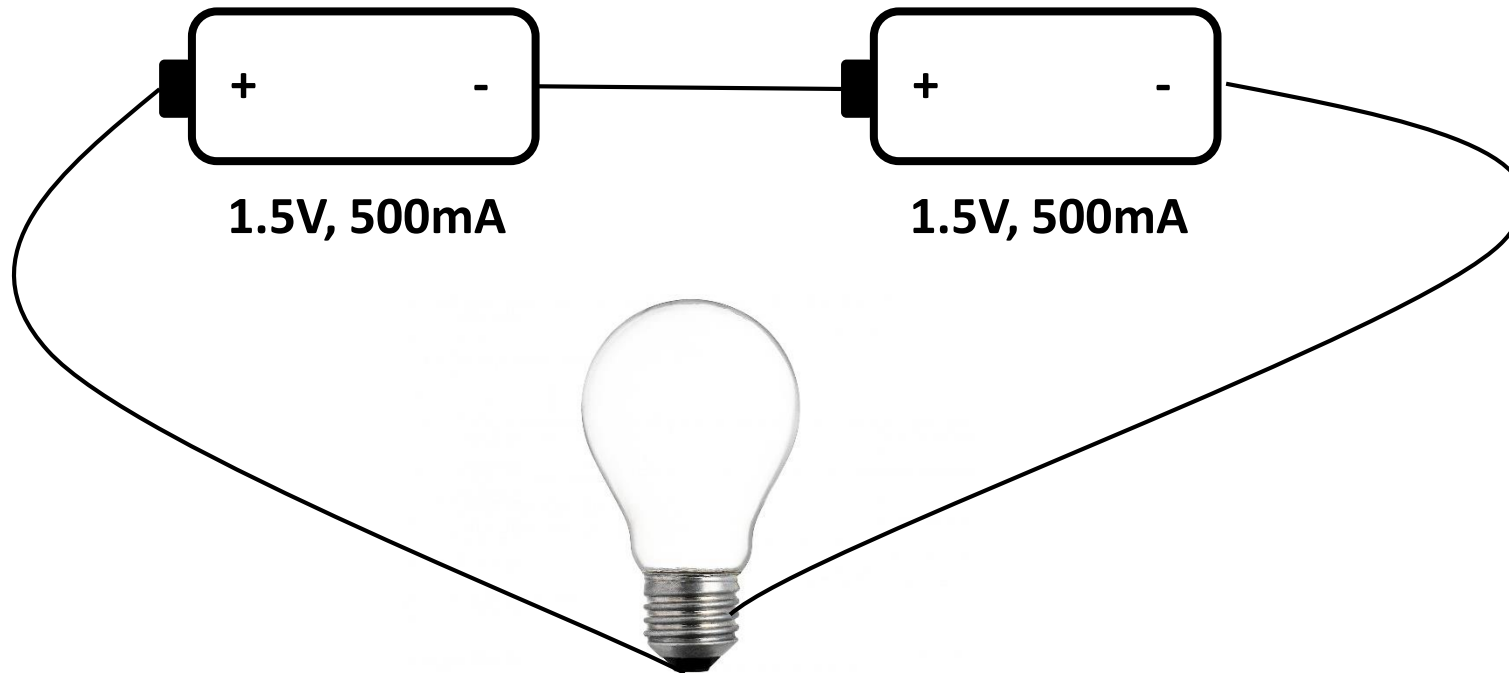

Circuit:
3V
500mA

AC vs. DC
considerations:


Do not Setup AC
circuits in series – as
they must remain a
constant voltage.

**Connected
from negative
to positive**

Solar Professorsm

Let's see it in action:
Batteries in Parallel

Circuit:
1.5V
1000mA (or 1A)

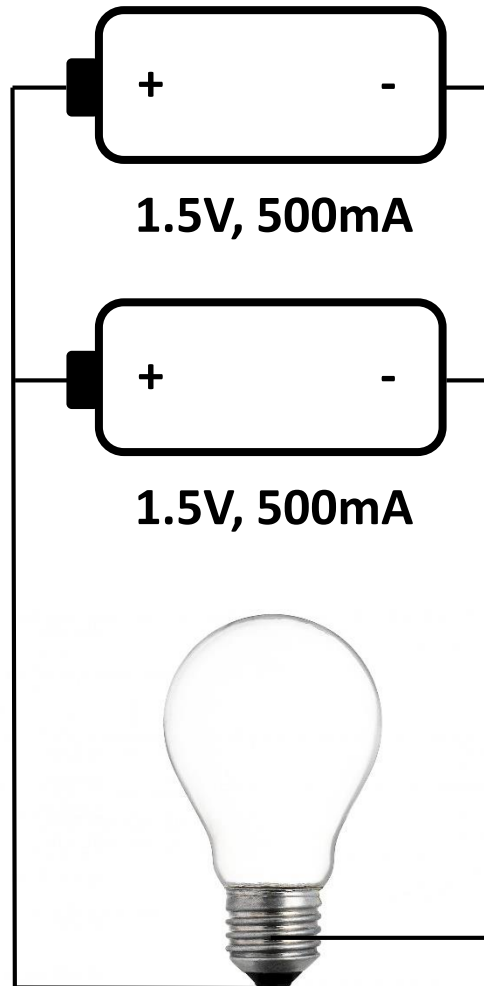


Series vs. Parallel

AC vs. DC
considerations:

AC circuits are typically
run in parallel (and are
called branch circuits).


**Connect all
positives and
all negatives to
load**

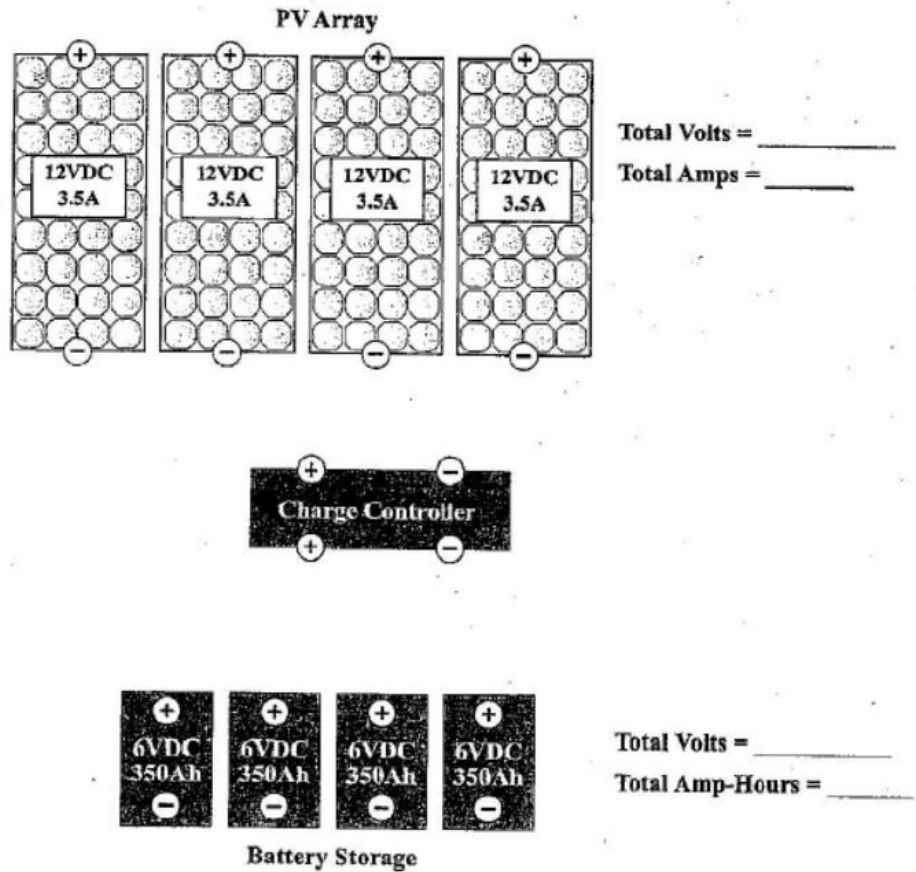Exercise B: DESIGN A 24V SYSTEM WITH FOUR 12V PV MODULES




PHOTOVOLTAICS: DESIGN AND INSTALLATION MANUAL

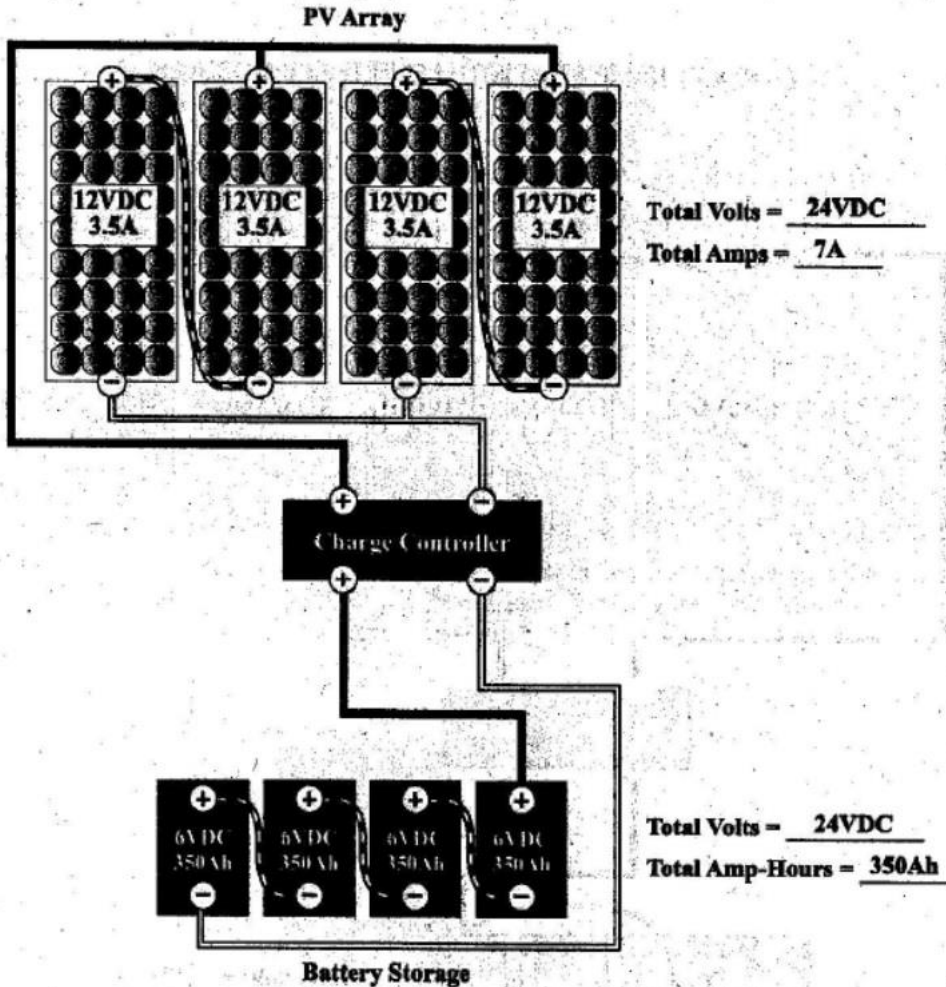
Answer B: 24V SYSTEM WITH FOUR 12V PV MODULES



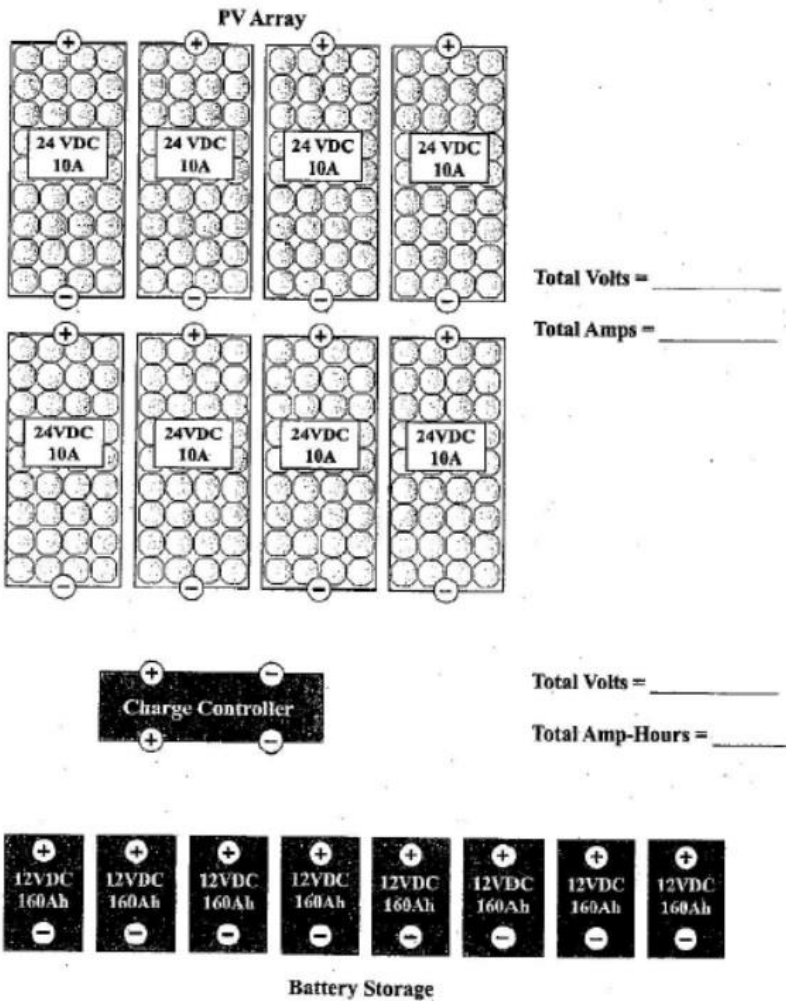Exercise D: DESIGN A 48V SYSTEM WITH EIGHT 24V PV MODULES



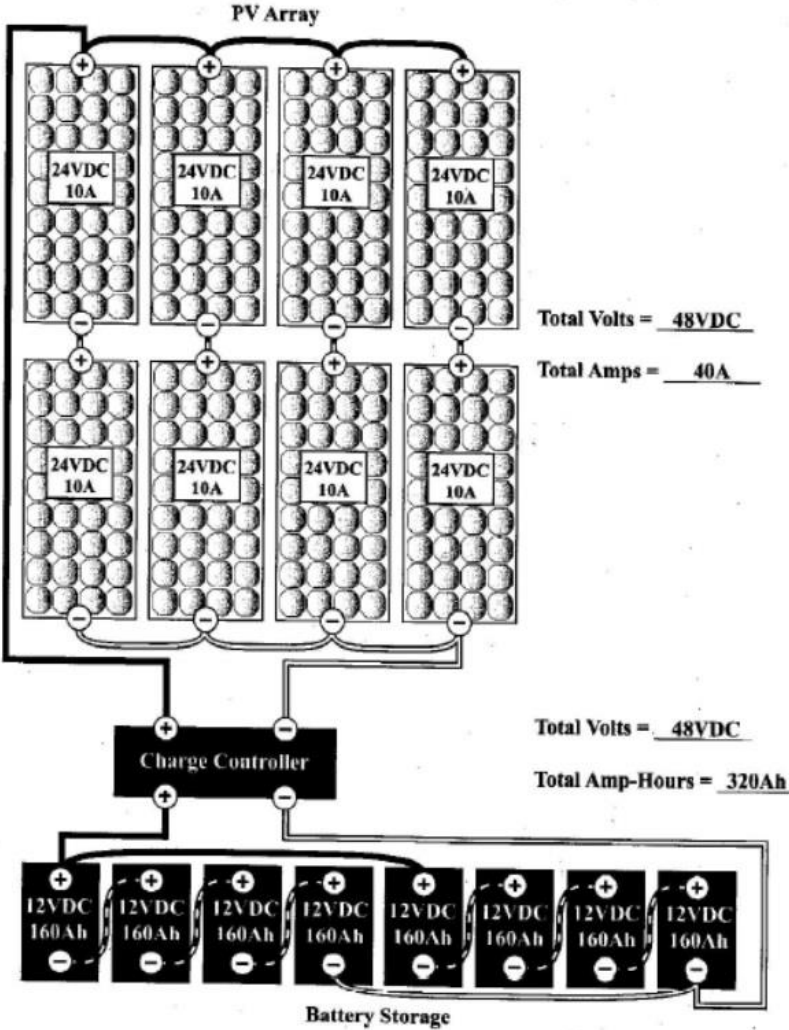Answer D: 48V SYSTEM WITH EIGHT 24V PV MODULES



SAMPLE NABCEP TYPE QUESTION

Q: There are 24 300W modules in a system. We can not exceed the 600V residential maximum for this string system. The specs of the modules are 40V VOC and 7A ISC. How should we design the system?

A: 2 strings of 12 modules. $40V \times 12 \text{ modules} = 480V$, $7A \times 2 \text{ strings} = 14A$.



Thank You

SolarProfessor.info